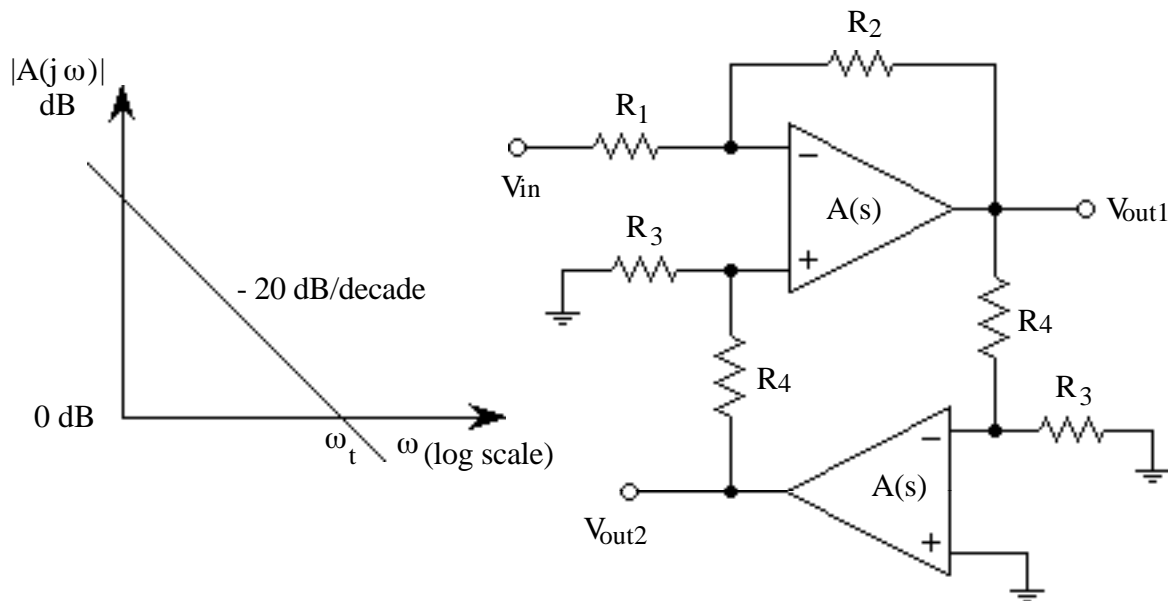


Note: in this question, certain symbols do not render properly in some PDF readers. I have annotated those.

Q.1 The circuit shown below is a second-order filter containing no capacitor external to the op amps (it is called an active-R biquad). Assume that the two op amps are identical with infinite input resistance, zero output resistance and open-loop gain  $A(s)$  as given by the Bode plot shown below.

- Obtain the transfer functions  $\frac{V_{out1}}{V_{in}}(s)$  in terms of R's and  $\omega_t$ . (omega\_t)
- Obtain expressions for  $\omega_o$  and Q and their sensitivities with respect to R's and  $\omega_t$ . (omega\_t)
- Use this circuit to realize a second-order bandpass filter with unity center-frequency gain, center frequency of 10 krad/sec and a BW of 1 krad/sec. Assume that the op amps have unity-gain-bandwidth ( $\omega_t$ ) of 10 Mrad/sec. Obtain all the resistors values.



- Q.2 (a) Using Mesh analysis write by inspection a set of mesh matrix equations (size 2 x 2) in the form  $[\mathbf{A}][\mathbf{I}] = \mathbf{V}$  for the circuit shown in Figure 2. Your final answer should contains numbers only in the  $\mathbf{A}$  matrix and the  $\mathbf{V}$  column vector.
- (b) Using the result in part (a) solve the voltage  $v$  across the  $4\ \Omega$  resistor.

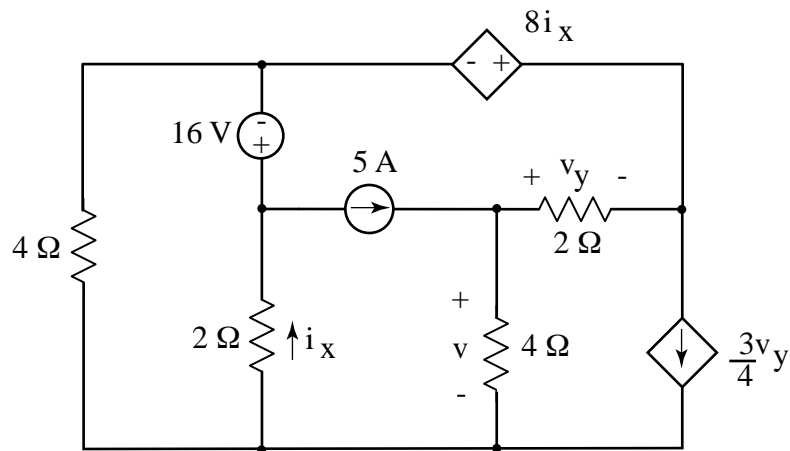


Figure 2

- Q.3 (a) Using any method of your choice determine the steady state current  $i_{out}(t)$  in the circuit shown in Figure 3 if  $v_s(t) = 12\cos(2t + 45^\circ)$  V.  $v_s(t) = 12\cos(2t+45\text{ deg})$
- (b) Determine the natural response of this circuit assuming the capacitor held an  $v_c(0^-) = V_0$  initial voltage of  $v_c(0^-) = V_0$  and the initial current through the inductor  $i_L(0^-) = I_0$ , respectively.  $i_L(0^-) = I_0$
- (c) If  $I_0 = -1\text{A}$  and  $V_0 = 2\text{V}$ , plot  $i_{out}(t)$  versus time.  $I_0 = -1\text{ A and } V_0 = 2\text{ V}$
- (d) Plot the asymptotic frequency response of this circuit if  $i_{out}$  is considered the output of the circuit and the independent source as the input.

- (e) If  $i_{out}$  is considered the output of the circuit and the independent source as the input, is this circuit reciprocal? Give a brief explanation for your reasoning.

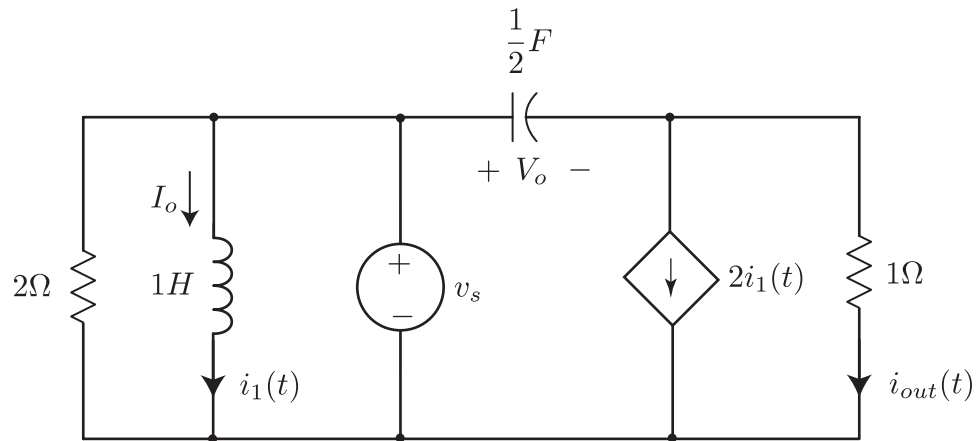


Figure 3

---

Q4. This question has 7 parts (a)-(g).

- (a) Draw a circuit diagram of a CMOS inverter.
- (b) Assume that  $\mu_n = 3\mu_p$ ,  $V_{dd} = 1.8 \text{ V}$ ,  $V_{tn} = |V_{tp}| = 0.5 \text{ V}$ ,  $\lambda = 0.1$ , and the width of NMOS is  $1 \mu\text{m}$ . Explain how you would select the size of the PMOS transistors such the threshold voltage of the inverter was  $1 \text{ V}$ ?
- (c) What are the  $V_{OH}$  and  $V_{OL}$  of the inverter designed in (b)
- (d) What capacitance does this inverter present to a preceding logical gate? Show your answer in terms of the small signal transistor capacitances.
- (e) What is the output capacitance of this inverter? Show your answer in terms of the small signal transistor capacitances.
- (f) What transistor width ratios would you select to make  $t_{pHL}$  equal to  $t_{pLH}$ ?
- (g) What transistor width ratios would you select to minimize the average time delay ( $t_p$ )?


- 
- Q5. Design a BJT differential amplifier that provides two single-ended outputs (at the collectors). The amplifier is to have a differential gain (to each of the two outputs) of at least 100 V/V, a differential input resistance  $\geq 10 \text{ k}\Omega$ , and a common-mode gain (to each of the two outputs) no greater than 0.1 V/V. Use a 2-mA current source for biasing. Give the complete circuit with component values and suitable power supplies that allow for  $\pm 2 \text{ V}$  swing at each collector. Specify the minimum value that the output resistance of the bias current source must have. The BJTs available have  $\beta \geq 100$ . What is the value of the input common-mode resistance when the bias source has the lowest acceptable resistance?

- 
- Q6. An npn BJT with grounded emitter is operated with  $V_{BE} = 0.700$  V, at which the collector current is 1 mA. A 10-k $\Omega$  resistor connects the collector to a +15 V supply. What is the resulting collector voltage  $V_C$ ? Now, if a signal applied to the base raises  $v_{BE}$  to 705 mV, find the resulting total collector current  $i_C$  and total collector voltage  $v_C$  using the exponential  $i_C - v_{BE}$  relationship. For this situation, what are  $v_{be}$  and  $v_c$ ? Calculate the voltage gain  $v_c/v_{be}$ . Compare with the value obtained using the small-signal approximation, that is,  $-g_m R_C$ .

Q7. This question has 2 parts (a)-(b). Part (a) has 2 subparts (i)-(ii) and part (b) has 3 subparts (i)-(iii).

(a) Consider the circuit shown below. It contains a potentiometer modeled by two variable resistors of value  $\alpha R$  and  $(1 - \alpha)R$  where  $\alpha$  is a variable  $0 \leq \alpha \leq 1$  and  $R = 3 \Omega$ . For the circuit, do the following:

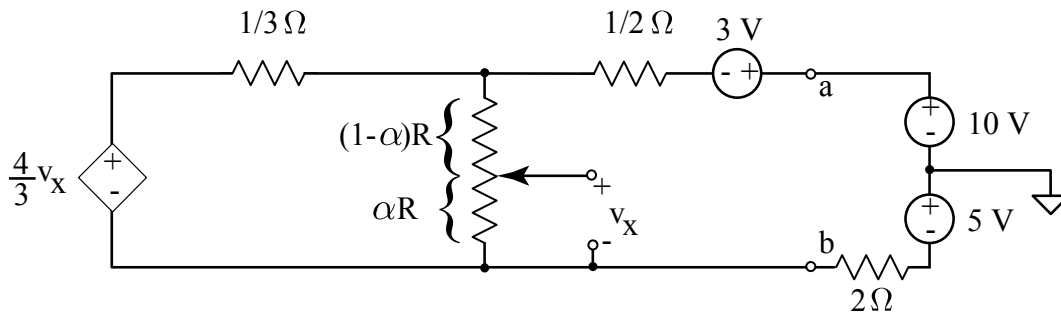
- i. Find the Thevenin equivalent of the circuit to the left of the nodes a-b.
- ii. Determine the value of  $\alpha$  for
  - A.  $R_{TH} = -1 \Omega$
  - B.  $R_{TH} = 1 \Omega$



(b) The network shown in the figure below has been in that state for a long time with the switches closed. At  $t = 0$ , the switches are simultaneously opened as indicated by the arrows. For this circuit using Laplace Transform techniques do the following;

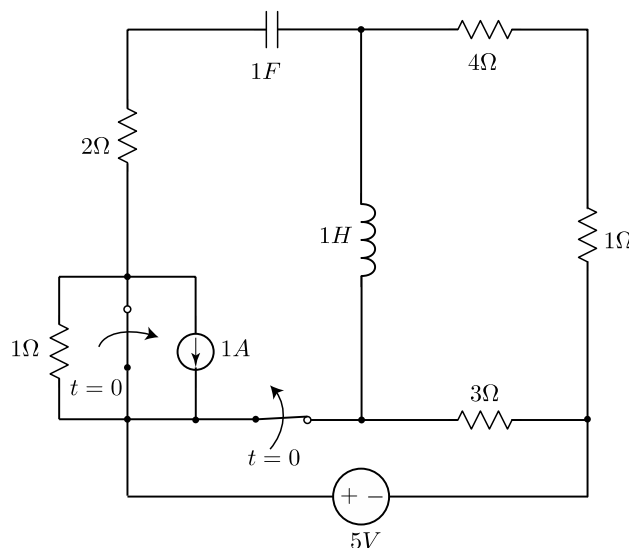- i. Determine the poles of this circuit for  $t \geq 0$ .
- ii. Determine the current  $i_c(t)$  through the capacitor for  $t \geq 0$ .
- iii. Using the final value theorem determine  $v_{4\Omega}(\infty)$ .

Tables of Laplace Transforms are given on the page following.



---

Table of Laplace Transforms

$f(t)$ for $t \geq 0$	$\mathcal{L}(s)$
$u(t)$	$\frac{1}{s}$
$e^{-at}u(t)$	$\frac{1}{s+a}$
$t^n u(t)$	$\frac{n!}{s^{n+1}} \quad (n = 0, 1, \dots)$
$\sin(\omega t)u(t)$	$\frac{\omega}{s^2 + \omega^2}$
$\cos(\omega t)u(t)$	$\frac{s}{s^2 + \omega^2}$
$e^{-at} \sin(\omega t)u(t)$	$\frac{\omega}{(s+a)^2 + \omega^2}$
$e^{-at} \cos(\omega t)u(t)$	$\frac{s+a}{(s+a)^2 + \omega^2}$
$e^{-at} \left[ C \cos(\omega t) + \frac{D - aC}{\omega} \sin(\omega t) \right] u(t)$	$\frac{Cs + D}{(s+a)^2 + \omega^2}$